

**FACULTY OF SCIENCE**

**M.Sc. II – Semester (New)(CBCS / Non-CBCS) Examination, April / May 2014**

**Subject: Physics & Applied Electronics  
Paper – V (205): Electronics – II**

**Time: 3 Hours**

**Max.Marks: 80**

**Note: Answer All questions from Part – A and Part – B.**

**Each question carries 4 marks in Part – A and 12 marks in Part – B.**

**PART – A (8 x 4 = 32 Marks)  
[Short Answer Type]**

- 1 List the characteristics of ideal operational amplifier. What is CMRR?
- 2 Explain an operational amplifier as an integrator.
- 3 Differentiate serial in serial out and serial in parallel out registers using suitable diagrams.
- 4 Explain Race around condition in flip-flops.
- 5 Distinguish between synchronous and asynchronous counters.
- 6 Define accuracy and resolution of A/D converter.
- 7 Write a short note on FLAG register in 8085 microprocessor.
- 8 Enumerate the addressing modes in 8085 microprocessor.

**PART – B (4x12 = 48 Marks)  
[Essay Answer Type]**

- 9 (a) Explain, how to generate a square wave using an operational amplifier using suitable diagram and derive an expression for its time period.  
**OR**  
(b) Discuss an op amp as the fundamental building block in an electronic analog computer.
- 10 (a) Minimize the following Boolean expressions:  
i)  $Y = A(A' + C)(A'B + C)(A'BC + C')$     ii)  $Y = \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$   
**OR**  
(b) Draw the circuit diagram of master-slave J.K. flip-flop using NAND gates and explain its working.
- 11 (a) Explain in detail A/D converter by successive approximation method and write its advantages and disadvantages.  
**OR**  
(b) Discuss decade counter using flip-flops with help of suitable timing diagram.
- 12 (a) Explain arithmetic and logic instructions of 8085  $\mu p$  with suitable examples.  
**OR**  
(b) Write an ALP to arrange given numbers in ascending order using 8085  $\mu p$  instructions.

\*\*\*\*